

a simple CMOS beta multiplier 1uA current source

- design review -


Rod Burt, Aug 8, 2024

design goals

- $i_{out} = 1\mu A$
- minimize i_{out} variations
 - PVT variations
 - Process corners ss, sf, ff, and fs
 - supply Voltage from 1.7V to 1.9V
 - Temperature from $-40^{\circ}C$ to $125^{\circ}C$
 - device mismatch
- minimize layout area

a simple CMOS beta multiplier 1uA current source

Rod Burt, Aug 8, 2024

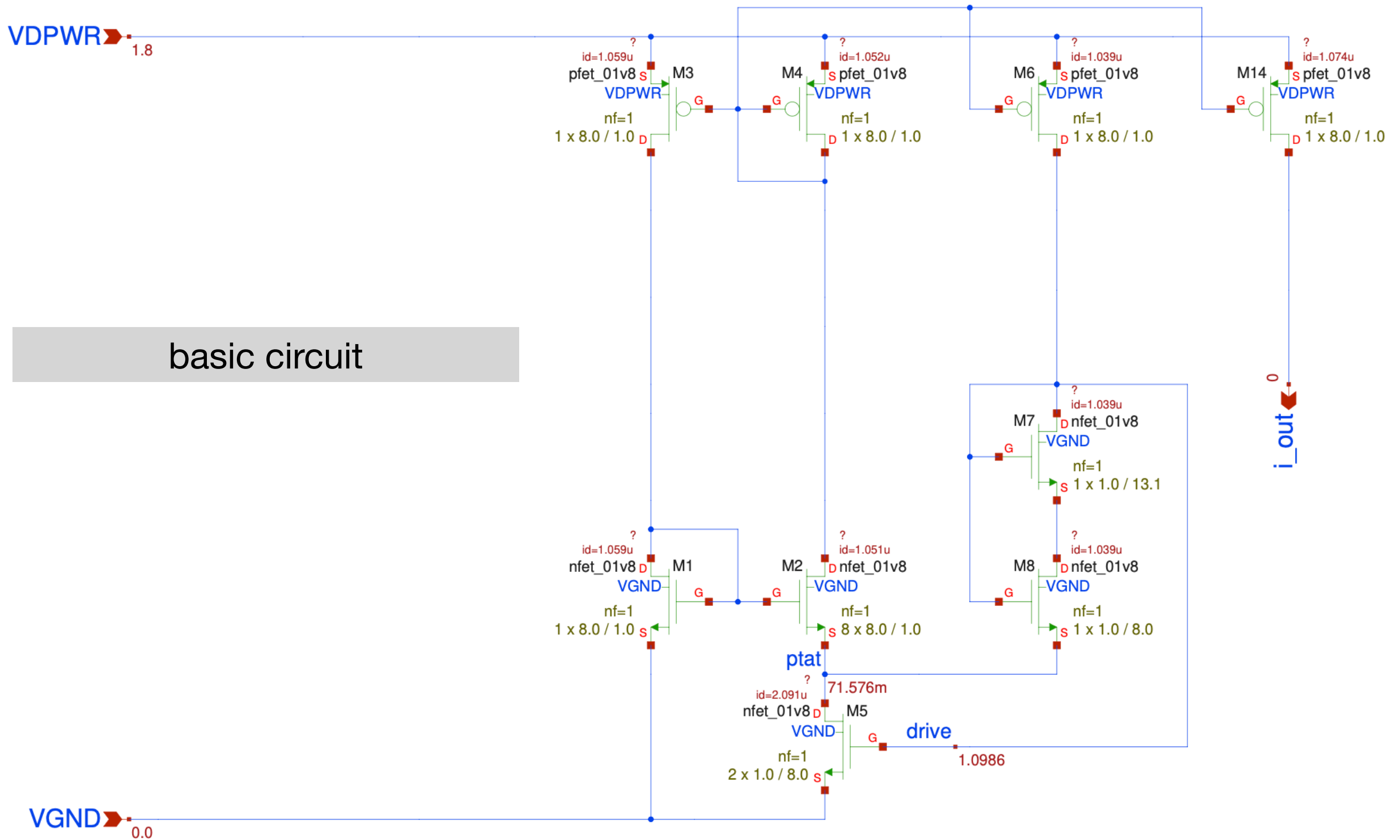

1st order analysis

PMOS devices M3, M4, M6, and M14 form a mirror setting all drain currents to i

NMOS devices M1 and M2 operate in subthreshold and form a beta multiplier setting $V_{ptat} = V_{gs1} - V_{gs2} \approx nV_t \ln(W/L \text{ ratio of } M2/M1)$, for a W/L ratio of $M2/M1 = 8$

$$V_{ptat} \approx n \frac{kT}{q} \ln(8)$$

$V_{drive} = V_{ptat} + V_{gs7,8}$ (composite device formed by M7 and M8)

$$V_{drive} \approx V_{ptat} + V_{th} + \sqrt{\frac{2i}{uCox \frac{W_{7,8}}{L_{7,8}}}}$$

NMOS device M5 operates in the triode region functioning as a resistor, thus

$$id5 \approx uCox \frac{W_5}{L_5} (V_{drive} - V_{th} - \frac{V_{ptat}}{2}) V_{ptat}$$

assuming


$$V_{gs7,8} \gg \frac{V_{ptat}}{2}$$

then

$$id5 \approx uCox \left(\frac{W_5}{L_5}\right)^2 \left(\frac{W_{7,8}}{L_{7,8}}\right) \left(n \frac{kT}{q} \ln(8)\right)^2$$


$$i \approx \frac{id5}{2}$$

multiplier 1uA current source

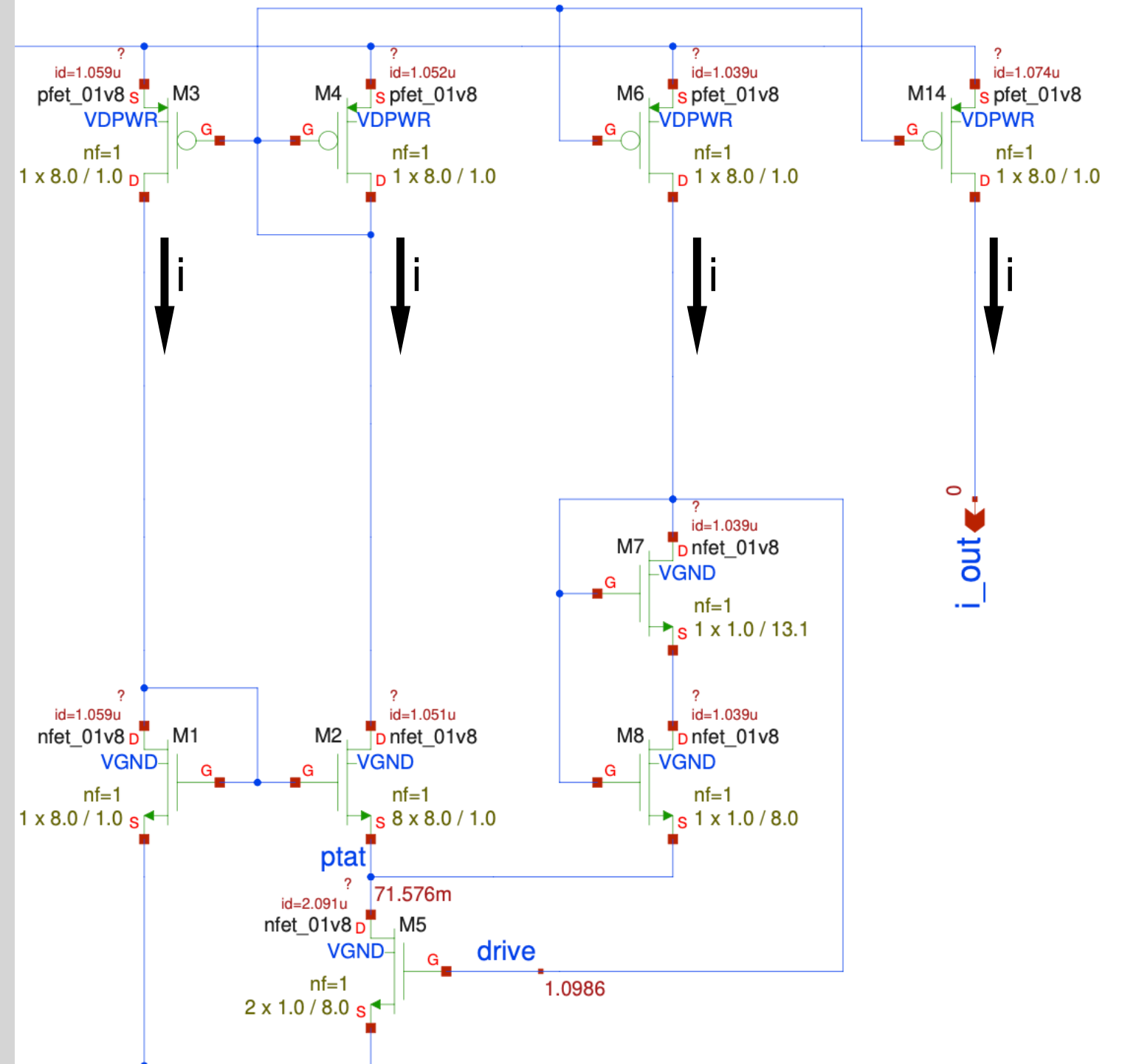


a simple CMOS beta multiplier 1uA current source

Rod Burt, Aug 8, 2024

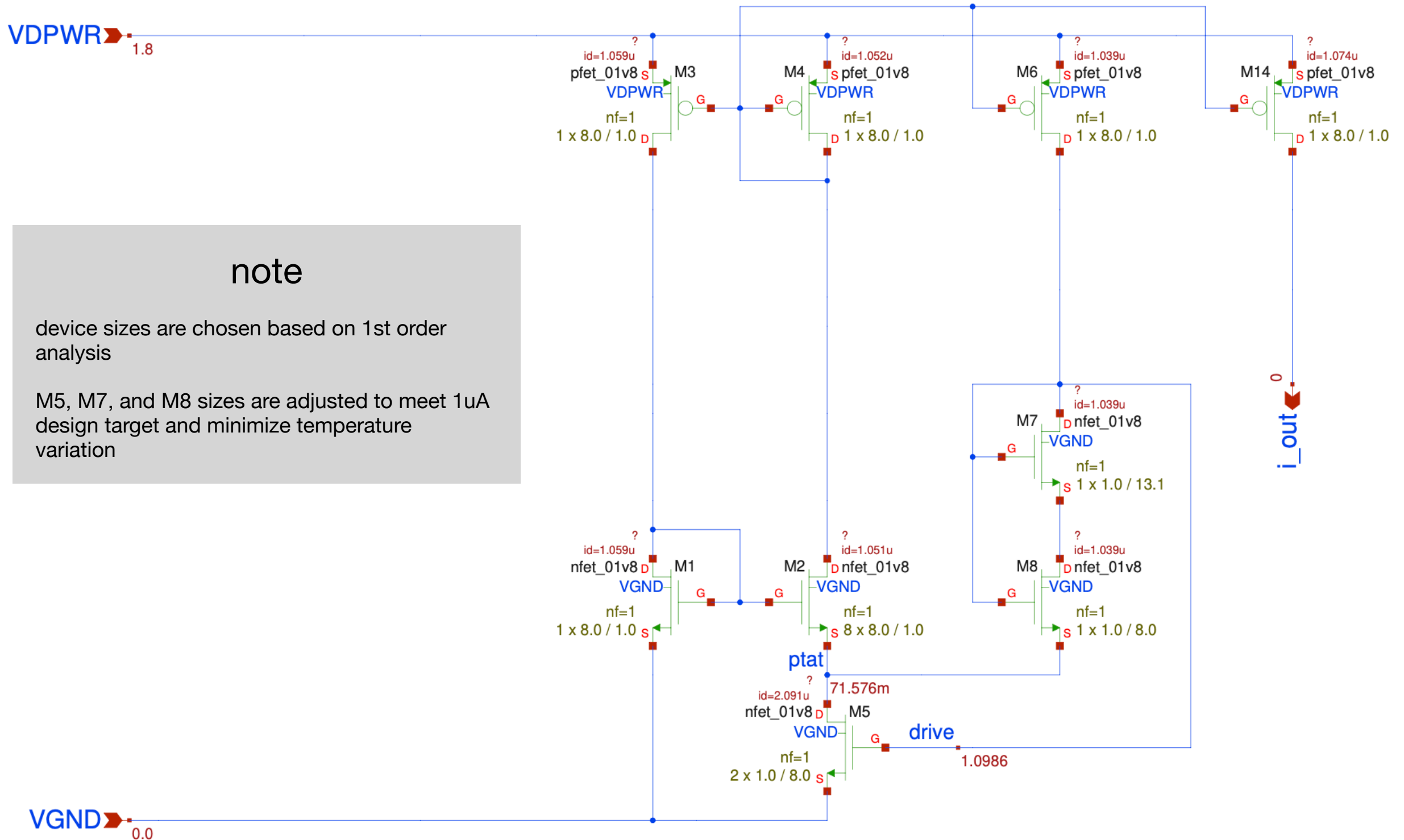

simulation of basic circuit

 


supply Voltage from 1.7V to 1.9V
 i_{out} variation $\approx \pm 2\%$


let's minimize this before we move on to other sims!

a simple CMOS beta multiplier 1uA current source

Rod Burt, Aug 8, 2024

 





simulation of circuit with cascodes

 

supply Voltage from 1.7V to 1.9V

i_{out} variation $\approx \pm 0.5\%$

simulation of circuit with cascodes

  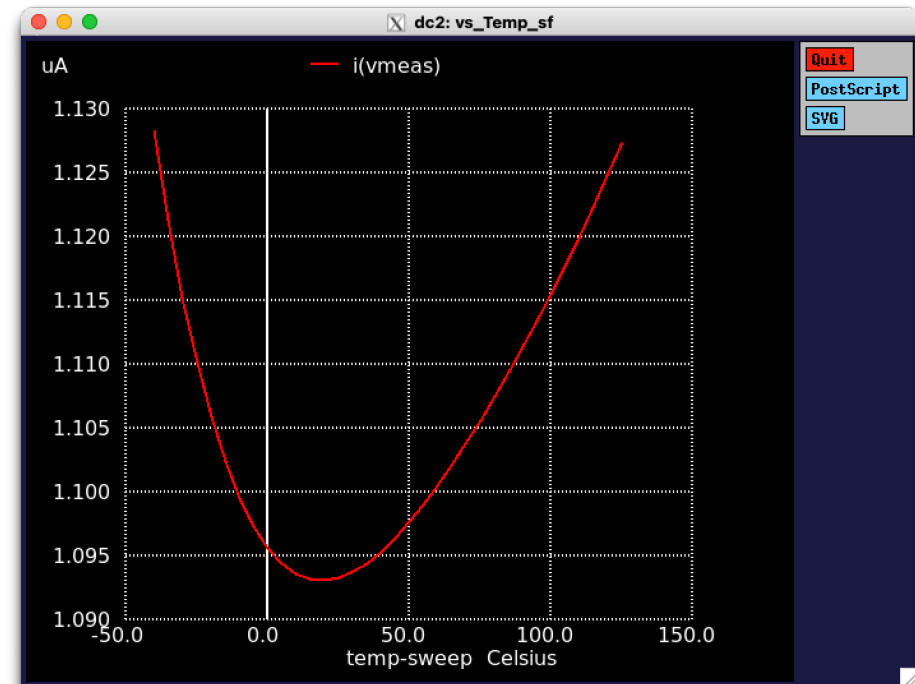 

Temperature from -40°C to 125°C and Process corners ss, sf, ff, and fs
 i_{out} variation $\approx \pm 10\%$

final considerations

- Start up


This circuit may have another valid operating point with all currents = 0. A start up circuit needs to be added to inject a small current to move the circuit into the desired state and then shut off the injected current so as not to add errors in normal operation.

- Stability

Any feedback loop has the potential to oscillate. This circuit has 2 loops involving the ptat and drive generation. To check for the potential of instability inject a small current pulse into the loops (the ptat node is ideal since it is part of both loops) and look for the level of ringing in the response.

a simple CMOS beta multiplier 1uA current source


Rod Burt, Aug 8, 2024

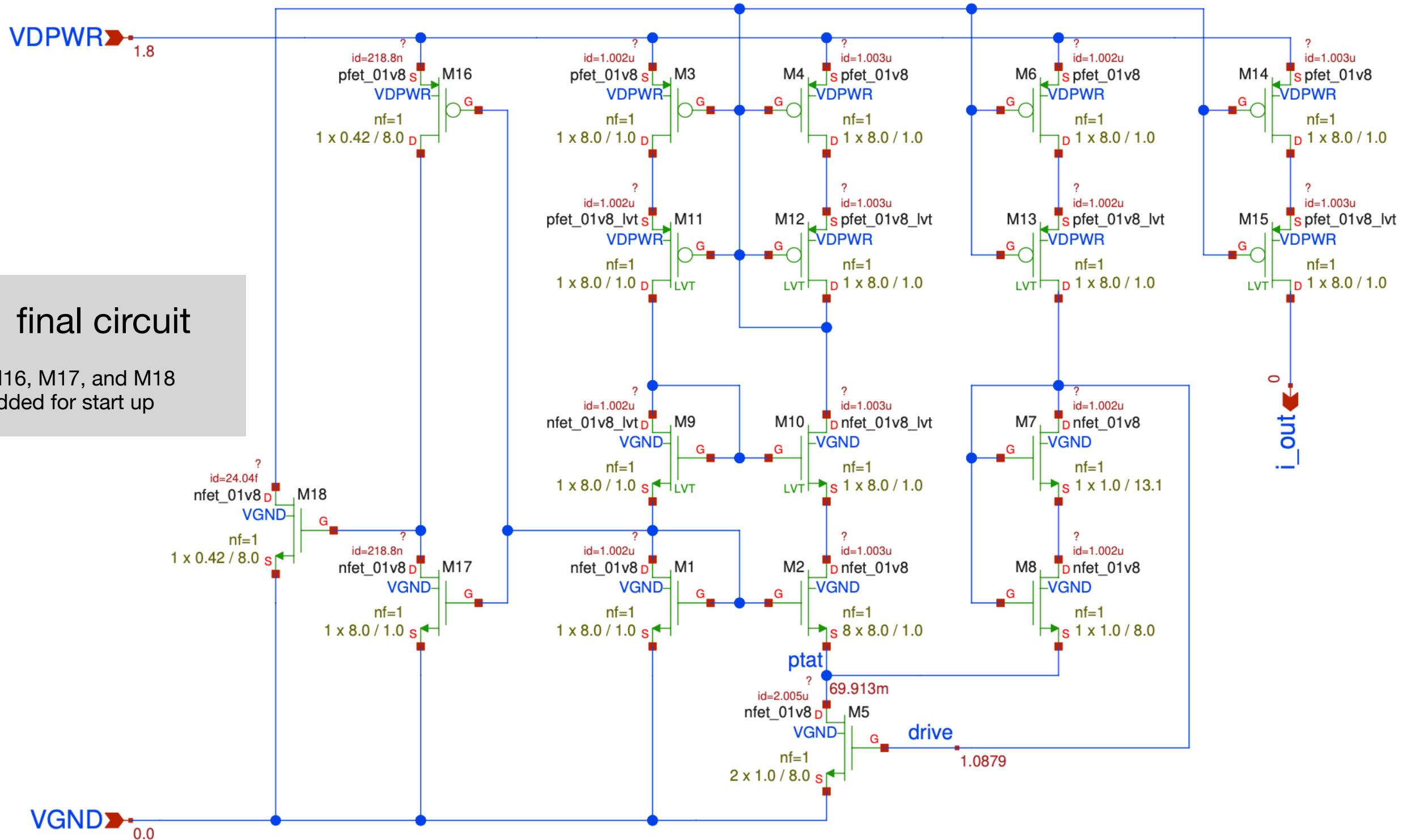

final circuit


M16, M17, and M18
added for start up

simulation of circuit with start up

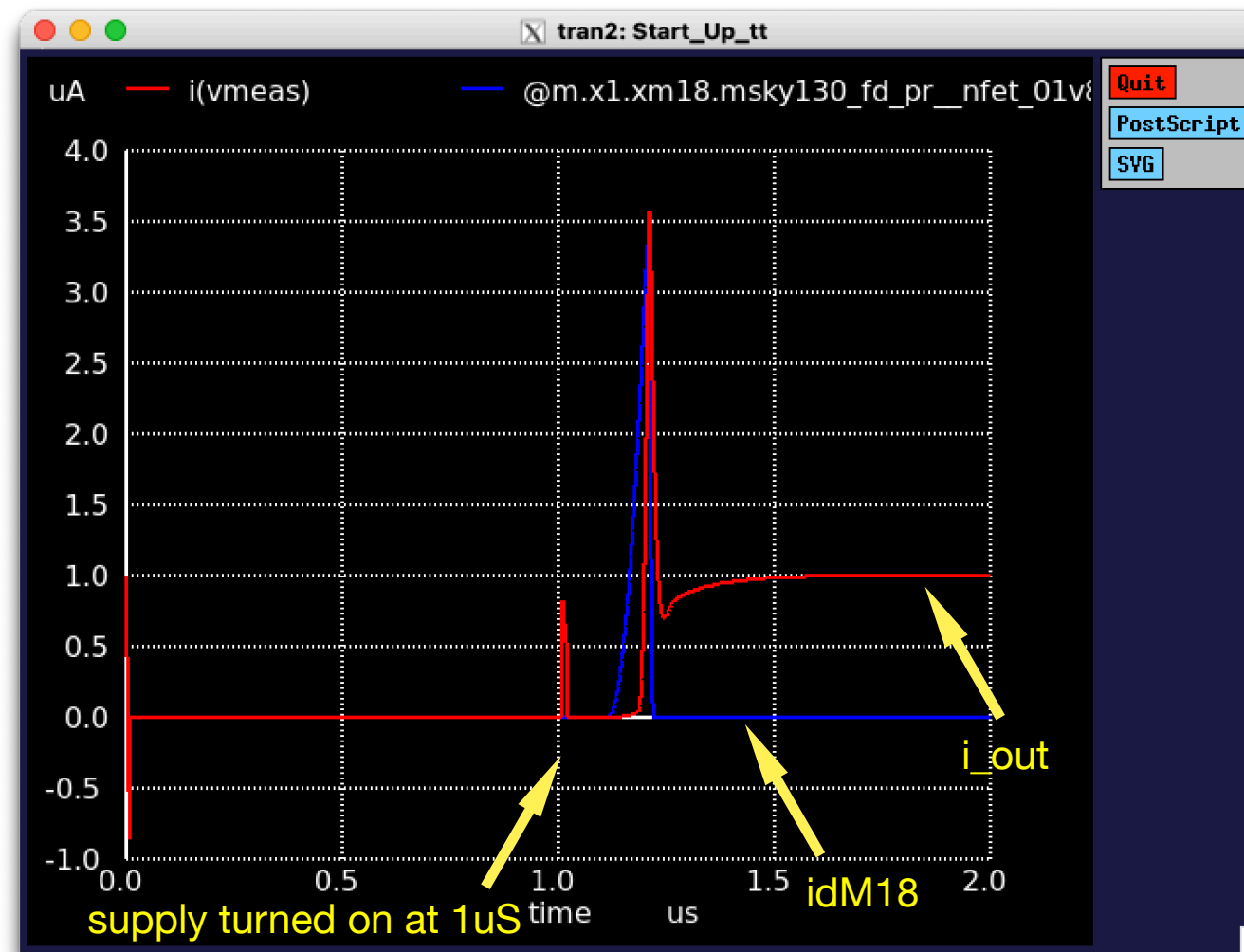

circuit starts up and M18 turns off

simulation to check stability

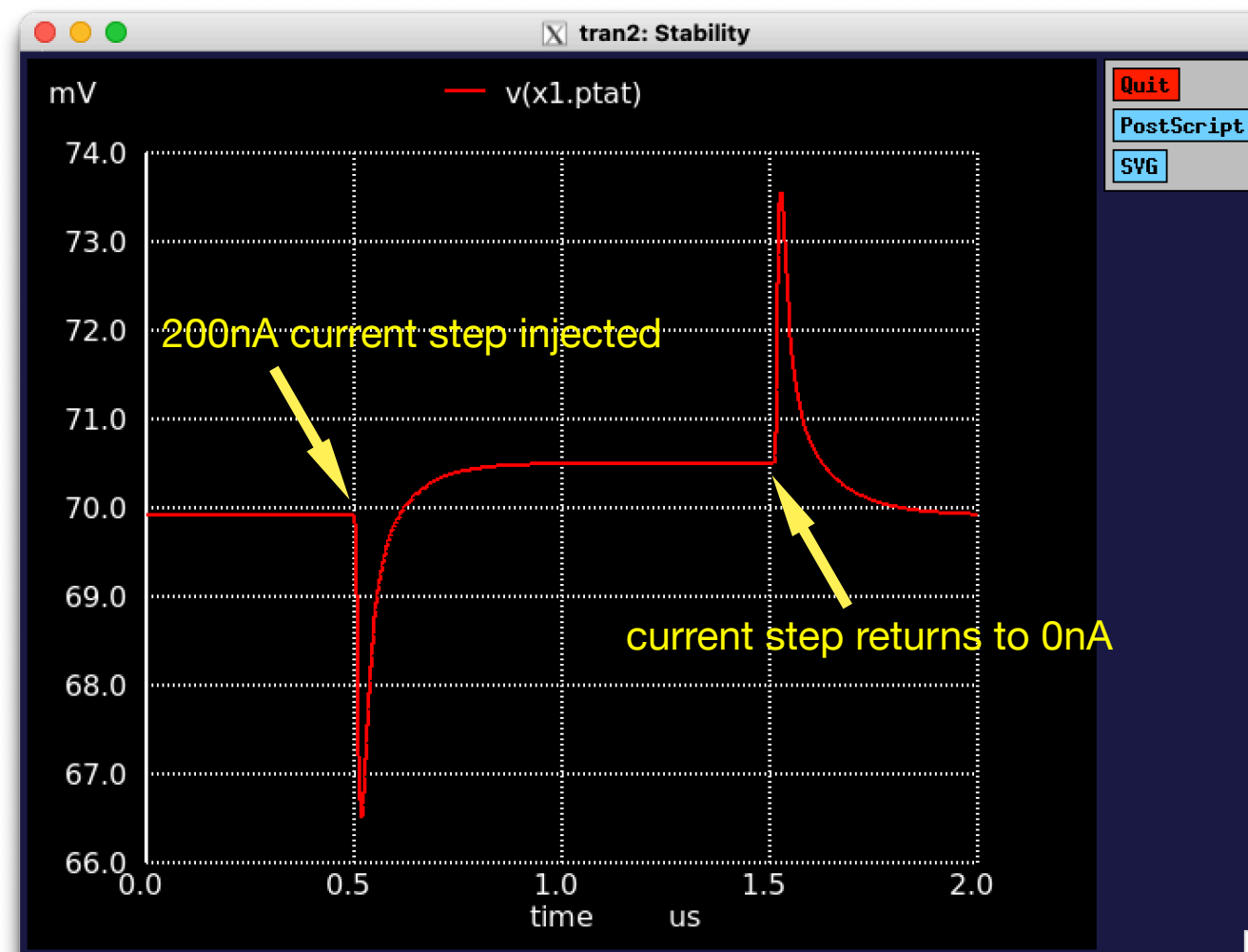

no overshoot in response indicates very good stability

layout considerations

- device matching

Match both W's and L's and create critical ratios with device multipliers.

Insure that everything the gate sees to the edge of it's well is the same.

Current flow from the source to the drain should be in the same direction.

For large ratios use some form of interdigitation. M1:M2's 1:8 ratio are laid out in a pattern of 4:1:4, 4 cells of M2:1 cell of M1:4 cells of M2.

- merging devices

Parametrized layout cells on the sky130A PDK allows merging of wells.

layout



layout area $\approx 38\mu\text{m} \times 22\mu\text{m}$

design goal results

- $i_{out} = 1\mu A$ ✓
- minimize i_{out} variations ✓
 - PVT variations $\approx \pm 10\%$
 - Process corners ss, sf, ff, and fs
 - supply Voltage from 1.7V to 1.9V
 - Temperature from $-40^{\circ}C$ to $125^{\circ}C$
 - device mismatch **still needs to be simulated with monti-carlo**
- minimize layout area ✓